

Name \_\_\_\_\_

EE 2240


**Exam #1**

Thursday, February 18, 2016

LIBR B32 and TAB 115, 2:30PM – 3:45PM


[closed book – one two-sided 8½"×11" page of notes and calculator allowed, nothing else]

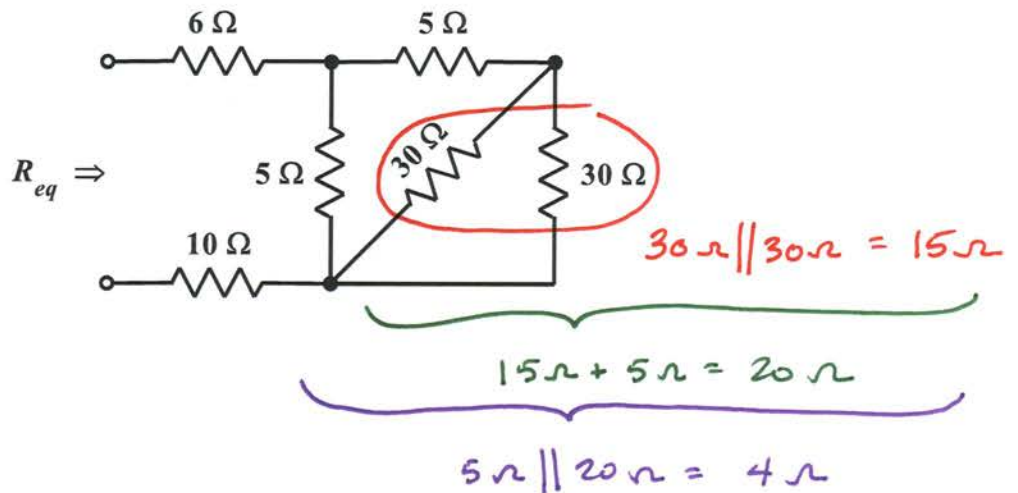1. [Equivalent Resistance] Determine the value of  $R_{eq}$  for the collection of resistors shown.



$$R_{eq} = 6\Omega + 4\Omega + 10\Omega = 20\Omega$$

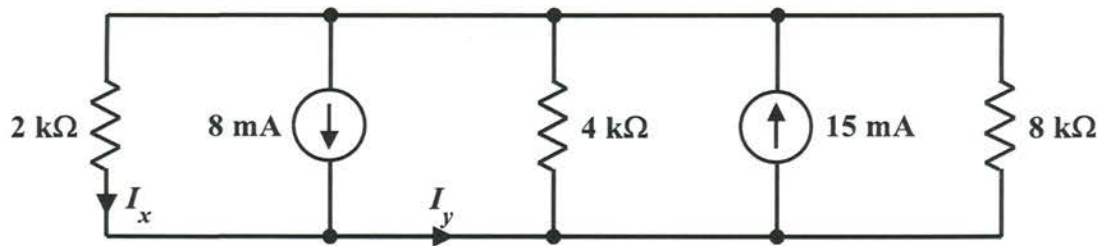
2. [Current Division] Determine the values of  $I_x$  and  $I_y$  in the circuit shown.



$$I_x = \frac{\frac{1}{2\text{ k}\Omega}}{\frac{1}{2\text{ k}\Omega} + \frac{1}{4\text{ k}\Omega} + \frac{1}{8\text{ k}\Omega}} \cdot (15\text{ mA} - 8\text{ mA}) = 4\text{ mA}$$

$$I_y = I_x + 8\text{ mA} = 12\text{ mA}$$

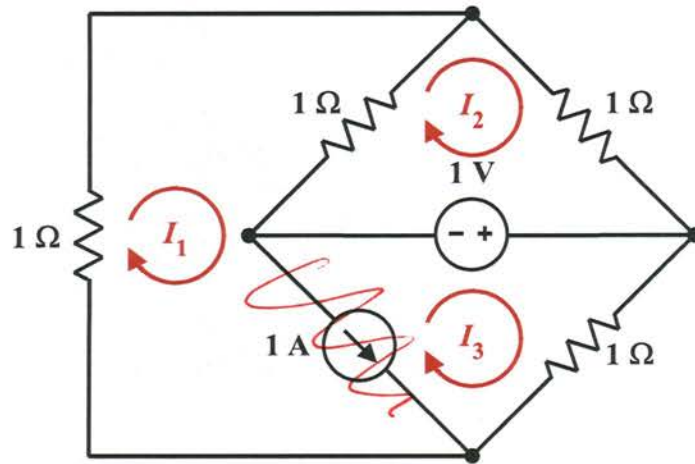3. [Mesh Analysis] Determine a set of equations that could be used to analyze the circuit shown by the mesh-analysis method, and express them in the standard matrix form. Use the mesh currents that are already assigned. *Do not attempt to solve the equations.*



$$I_1 - I_3 = 1A \quad (\text{constraint})$$

$$1\Omega(I_2 - I_1) + 1\Omega(I_2) + 1V = 0 \quad (\text{KVL for mesh 2})$$


$$1\Omega(I_1) + 1\Omega(I_1 - I_2) - 1V + 1\Omega(I_3) = 0$$

(KVL for supermesh 1,3)

In matrix form:

$$\begin{bmatrix} 1 & 0 & -1 \\ -1 & 2 & 0 \\ 2 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \\ 1 \end{bmatrix}$$

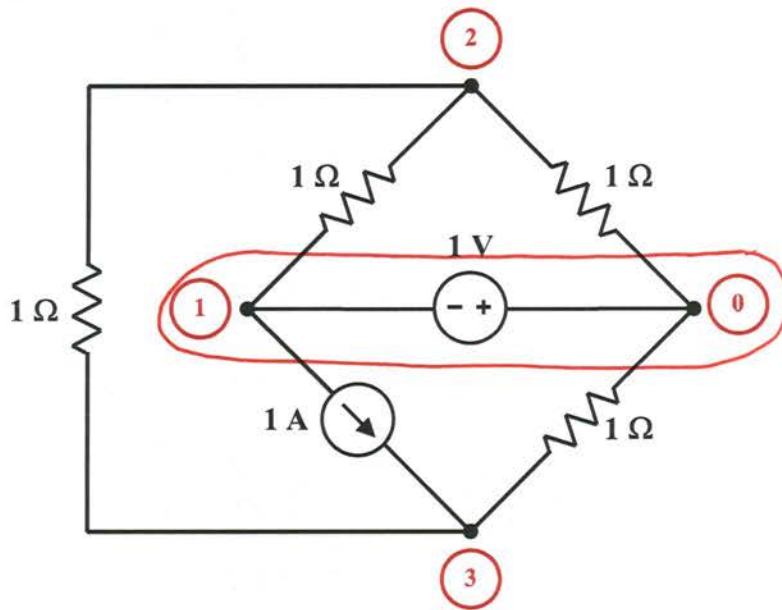4. [Nodal Analysis] Determine a set of equations that could be used to analyze the circuit shown by the nodal-analysis method, and express them in the standard matrix form. Use the node labels that are already assigned. **Do not attempt to solve the equations.**



$$V_1 = -1V \quad (\text{constraint})$$

$$\frac{V_2 - V_3}{1\Omega} + \frac{V_2 - V_1}{1\Omega} + \frac{V_2}{1\Omega} = 0 \quad (\text{KCL for node 2})$$

$$\frac{V_3 - V_2}{1\Omega} - 1A + \frac{V_3}{1\Omega} = 0 \quad (\text{KCL for node 3})$$

In matrix form:

$$\begin{bmatrix} 1 & 0 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -1 \\ 0 \\ 1 \end{bmatrix}$$

5. A set of simultaneous linear equations is given in standard matrix form below. Use any method to determine the numerical value of  $z$ . **Check your solution; there will be very little partial credit on this problem.**

$$\begin{bmatrix} 1 & 2 & 1 \\ 2 & 2 & 3 \\ 4 & 4 & 7 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 8 \\ 23 \\ 53 \end{bmatrix}$$

From row 3:  $4x + 4y + 7z = 53$  (1)

From row 2:  $2x + 2y + 3z = 23$  (2)

or  $4x + 4y + 6z = 46$  (3)

Subtract (3) from (1):

$$z = 7$$