

Name \_\_\_\_\_



EE 2240

**Exam #2**

Thursday, March 31, 2016


2:30PM – 3:45PM

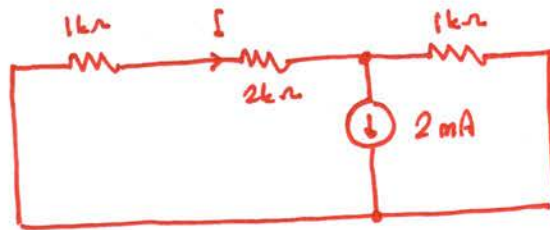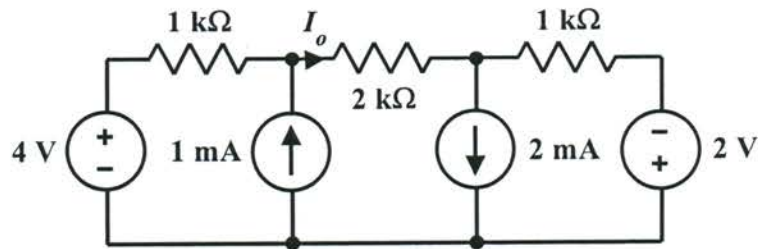1. [Superposition] Suppose you have decided to use the superposition method to solve for the value of  $I_o$  in the circuit shown below. As a first step, you want to solve for the contribution due to the 2mA independent current source. Show your work and determine this contribution. *You are not required to find the value of  $I_o$ , but just to determine the contribution due to the 2mA current source.*



$$I = \frac{1k\Omega}{3k\Omega + 1k\Omega} (2mA) = \frac{1}{2} mA$$

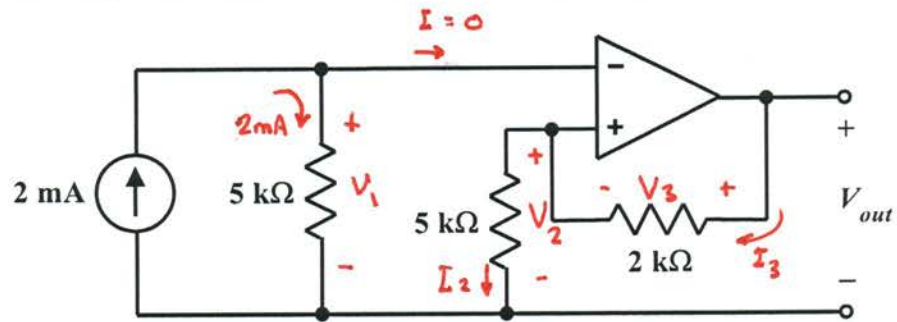2. [Operational Amplifier Circuit] Find the output voltage,  $V_{out}$ , of the circuit shown below:



$$V_1 = (5 \text{ k}\Omega)(2 \text{ mA}) = 10 \text{ V}$$

$$V_2 = V_1 = 10 \text{ V}$$


$$I_2 = \frac{V_2}{5 \text{ k}\Omega} = 2 \text{ mA}$$

$$I_3 = I_2 = 2 \text{ mA}$$

$$V_3 = (2 \text{ k}\Omega) I_3 = 4 \text{ V}$$

$$V_{out} = V_3 + V_2 = 14 \text{ V}$$

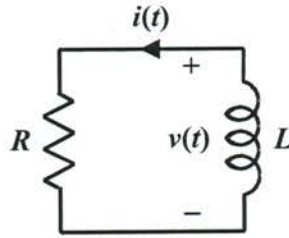3. [RL Circuit] In the circuit shown below,  $v(t) = 10e^{-2t}$  V and  $i(t) = 2e^{-2t}$  A.




- (a) Determine the value of  $R$ .

$$v(t) = R i(t) \Rightarrow R = \frac{v(t)}{i(t)} = \frac{10e^{-2t} \text{ V}}{2e^{-2t} \text{ A}} = 5 \Omega$$

- (b) Determine the value of  $L$ .


$$v(t) = -L \frac{di}{dt} \Rightarrow L = -\frac{v(t)}{\left(\frac{di}{dt}\right)} = -\frac{10e^{-2t} \text{ V}}{-4e^{-2t} \text{ A/s}} = 2.5 \text{ H}$$

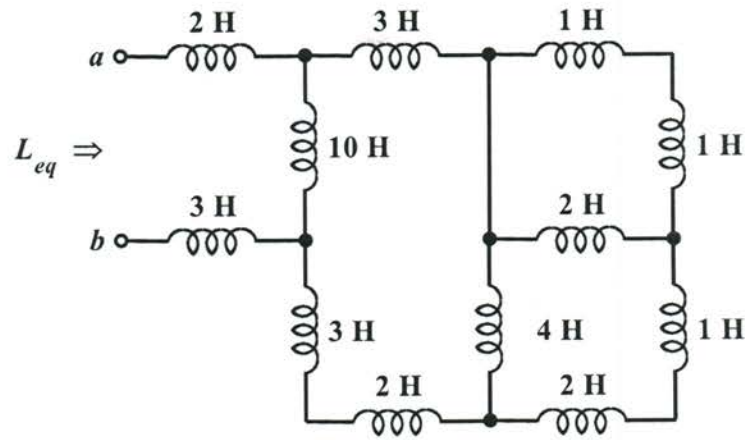4. [Capacitance/Inductance] Determine the equivalent inductance with respect to terminals  $a$ - $b$ .



$$L_{eq} = 10 \text{ H}$$

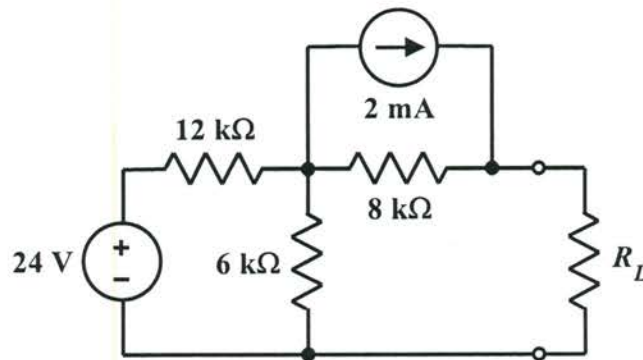5. [Maximum Power Transfer Theorem] For the circuit shown below:



(a) Find the value of the load resistance  $R_L$  needed for maximum power transfer to the load.

$$\begin{aligned}
 R_L &= 8\text{ k}\Omega + (12\text{ k}\Omega \parallel 6\text{ k}\Omega) \\
 &= 8\text{ k}\Omega + 4\text{ k}\Omega \\
 &= 12\text{ k}\Omega
 \end{aligned}$$

(b) For  $R_L$  equal to the value determined in part (a), find the power delivered to the load.

$$\begin{aligned}
 V_T &= (8\text{ k}\Omega)(2\text{ mA}) + \left( \frac{6\text{ k}\Omega}{12\text{ k}\Omega + 6\text{ k}\Omega} \right) (24\text{ V}) \\
 &= 16 + 8 = 24\text{ V}
 \end{aligned}$$

$$\therefore P_L = \frac{\left( \frac{24}{2} \right)^2}{12\text{ k}\Omega} = 12\text{ mW}$$