

Name \_\_\_\_\_

EE 2240

**Exam #3**


Wednesday, April 5, 2017

LIBR B07/B13 and TAB 115, 9:00AM – 9:50AM


[closed book – one one-sided 8½”×11” page of notes and calculator allowed, nothing else]

Work must be shown in a neat and orderly fashion if you expect to receive partial credit.

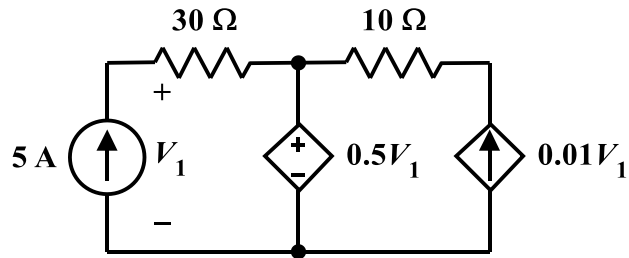1. Determine whether the dependent voltage source *delivers* or *absorbs* power, and how much.



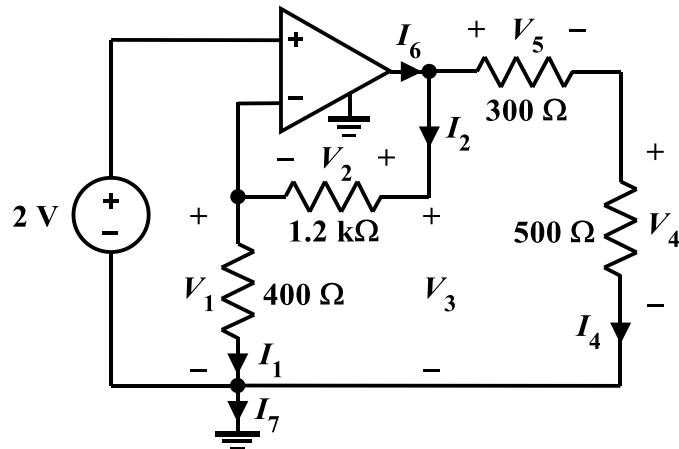2. The Op Amp shown in the circuit below is ideal.



Determine the following. Show your work and indicate proper units for each answer.

a.  $V_1 =$  \_\_\_\_\_

b.  $I_1 =$  \_\_\_\_\_

c.  $I_2 =$  \_\_\_\_\_

d.  $V_2 =$  \_\_\_\_\_

e.  $V_3 =$  \_\_\_\_\_

f.  $V_4 =$  \_\_\_\_\_



g.  $I_4 =$  \_\_\_\_\_

h.  $V_5 =$  \_\_\_\_\_

i.  $I_6 =$  \_\_\_\_\_

j.  $I_7 =$  \_\_\_\_\_

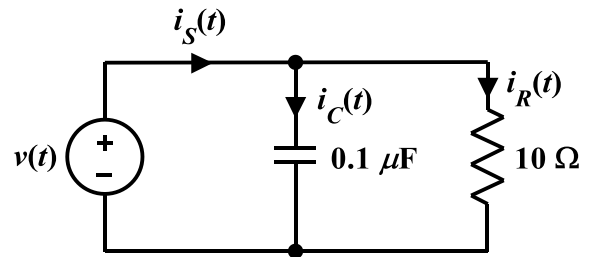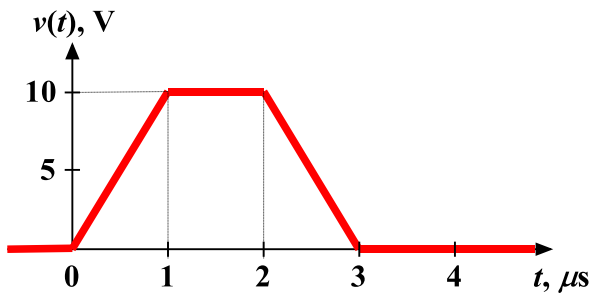3. Consider the circuit shown below. The voltage of the independent voltage source is given graphically, as shown.



- a. Accurately sketch the current through the capacitor,  $i_C(t)$ .
- b. Accurately sketch the current through the resistor,  $i_R(t)$ .
- c. Accurately sketch the current through the independent voltage source,  $i_S(t)$ .

4. If  $v_1(0) = 10\text{V}$ , determine  $v_2(t)$  for  $t \geq 0$ .

