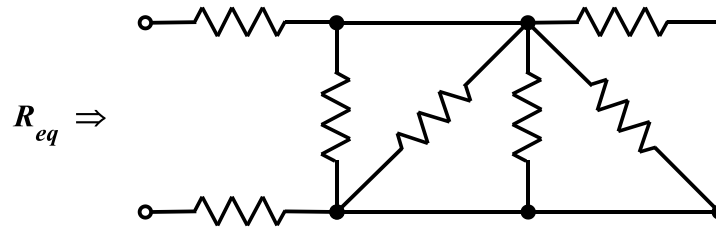


EE 2240  
**Homework Problem #006**



Each resistor is  $25 \Omega$ . Determine the value of  $R_{eq}$ .