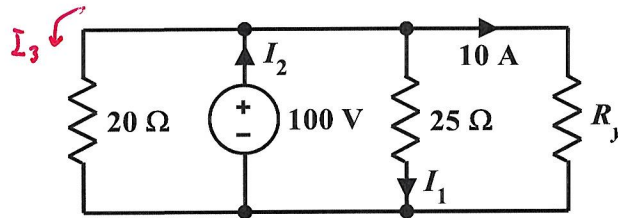


EE 2240  
Homework Problem #010

For the circuit shown below:



a. Determine the value of  $I_1$ .

$$I_1 = \frac{100\text{ V}}{25\ \Omega} = 4\text{ A}$$

b. Determine the value of  $R_y$ .

$$(10\text{ A})R_y = 100\text{ V} \Rightarrow R_y = \frac{100\text{ V}}{10\text{ A}} = 10\ \Omega$$

c. Determine the value of  $I_2$ .

$$I_3 = \frac{100\text{ V}}{20\ \Omega} = 5\text{ A}$$

$$I_2 = I_3 + I_1 + 10\text{ A} = 19\text{ A}$$

d. How much power does  $R_y$  absorb?

$$P_y = (100\text{ V})(10\text{ A}) = 1000\text{ W} = 1\text{ kW}$$

e. How much power does the independent voltage source deliver?

$$P_s = (100\text{ V})I_2 = (100\text{ V})(19\text{ A}) \\ = 1900\text{ W} = 1.9\text{ kW}$$