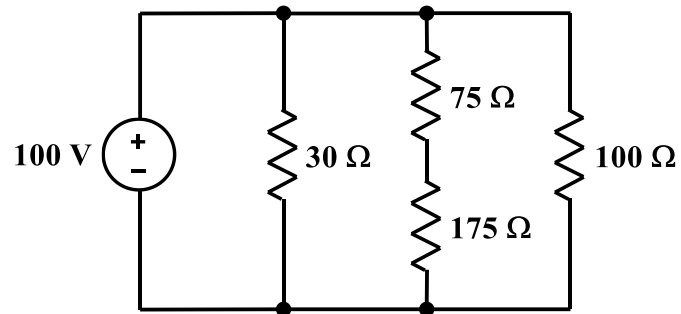


EE 2240
Homework Problem #015



How much power is the 75 Ω resistor absorbing?