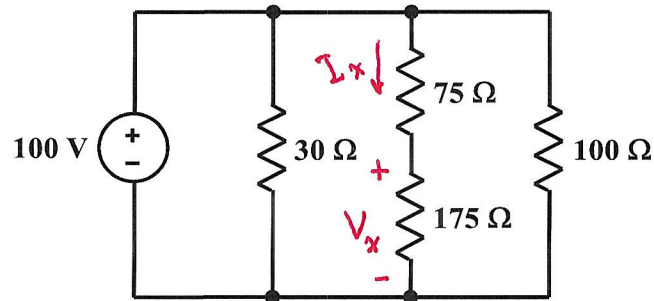


EE 2240
Homework Problem #015



How much power is the 75 Ω resistor absorbing?

$$V_x = \frac{75\Omega}{75\Omega + 175\Omega} \cdot 100V \quad (\text{Voltage Divider})$$
$$= 30V$$

$$P_x = \frac{V_x^2}{75\Omega} = \frac{(30)^2}{75} = 12W$$

$$\text{or } I_x = \frac{100V}{75\Omega + 175\Omega} = 0.4A \quad (\text{Ohm's Law})$$

$$P_x = I_x^2 (75\Omega) = (0.4)^2 (75) = 12W$$

$$\text{or } P_x = V_x I_x = (30)(0.4) = 12W$$