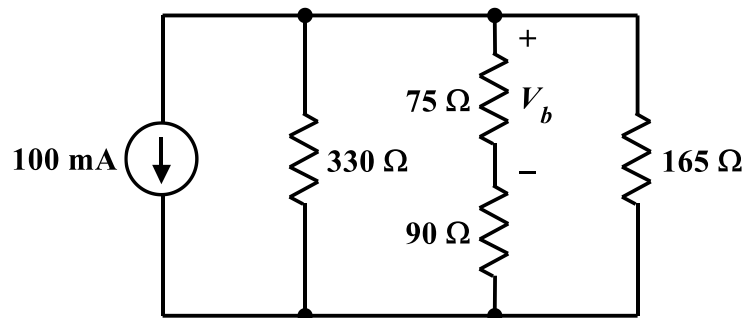


EE 2240
Homework Problem #025



Use the nodal analysis method to determine the value of V_b .