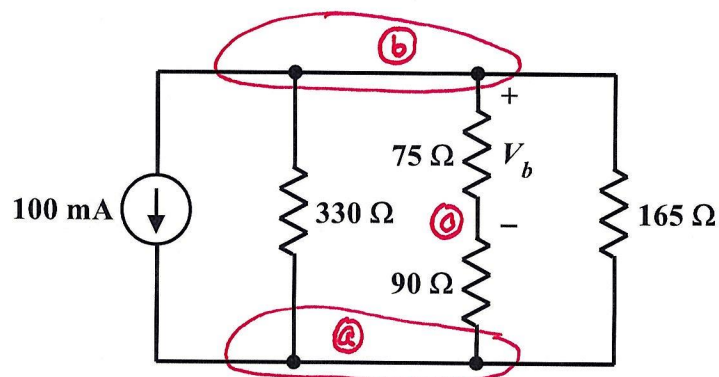


EE 2240  
**Homework Problem #025**



Use the nodal analysis method to determine the value of  $V_b$ .

$$-100 \text{ mA} + \frac{V_a - V_b}{330 \Omega} + \frac{V_a}{90 \Omega} + \frac{V_a - V_b}{165 \Omega} = 0 \quad (\text{KCL at node a})$$

$$100 \text{ mA} + \frac{V_b - V_a}{330 \Omega} + \frac{V_b}{75 \Omega} + \frac{V_b - V_a}{165 \Omega} = 0 \quad (\text{KCL at node b})$$

In matrix form:

$$\begin{bmatrix} \frac{1}{330} + \frac{1}{90} + \frac{1}{165} & -\frac{1}{330} - \frac{1}{165} \\ -\frac{1}{330} - \frac{1}{165} & \frac{1}{330} + \frac{1}{75} + \frac{1}{165} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 100 \times 10^{-3} \\ -100 \times 10^{-3} \end{bmatrix}$$

Solving yields  $V_b = -3 \text{ V}$

(see next page for  
 MATLAB solution)

```
>> a=[1/330+1/90+1/165 -1/330-1/165; -1/330-1/165 1/330+1/75+1/165]
```

```
a =
```

```
0.0202 -0.0091  
-0.0091 0.0224
```

```
>> c=[100e-3; -100e-3]
```

```
c =
```

```
0.1000  
-0.1000
```

```
>> b=a\c
```

```
b =
```

```
3.6000  
-3.0000
```