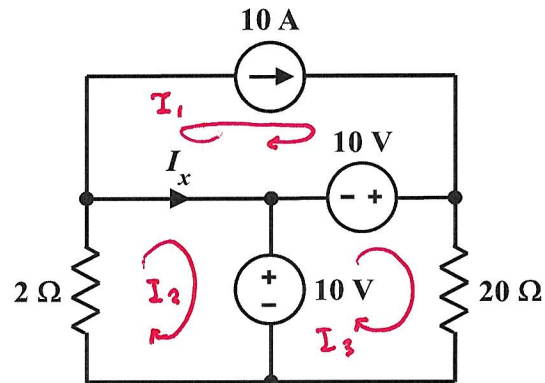


EE 2240
Homework Problem #030

- a. Assign mesh currents and express the mesh equations in the matrix form discussed in class.



$$\begin{aligned}
 I_1 &= 10 \text{ A} \\
 2I_2 + 10 \text{ V} &= 0 \\
 -10 \text{ V} - 10 \text{ V} + 20I_3 &= 0
 \end{aligned}$$

In matrix form:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 2 & 0 \\ 0 & 0 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -10 \\ 20 \end{bmatrix}$$

- b. Use MATLAB to solve the equations and determine the value of I_x . Show your work.

See the next page.

$$I_x = -15 \text{ A}$$

```
>> A=[1 0 0; 0 2 0; 0 0 20]
```

```
A =
```

```
1 0 0  
0 2 0  
0 0 20
```

```
>> c=[10 -10 20]'
```


```
c =
```

```
10  
-10  
20
```

```
>> b=A\c
```

```
b =
```

```
10  
-5  
1
```

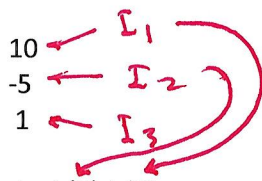

```
>> lx=b(2)-b(1)
```

```
lx =
```

```
-15
```

```
>>
```