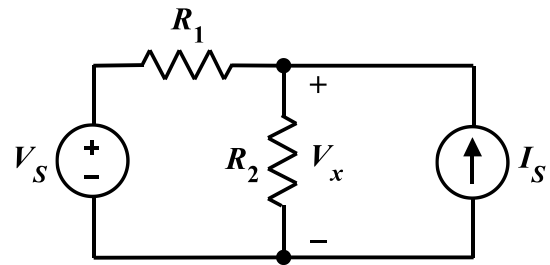


EE 2240  
**Homework Problem #032**



$V_x$  can be described by the equation

$$V_x = \alpha I_S + \beta V_S$$

Determine  $\alpha$  and  $\beta$  in terms of the resistor values.