
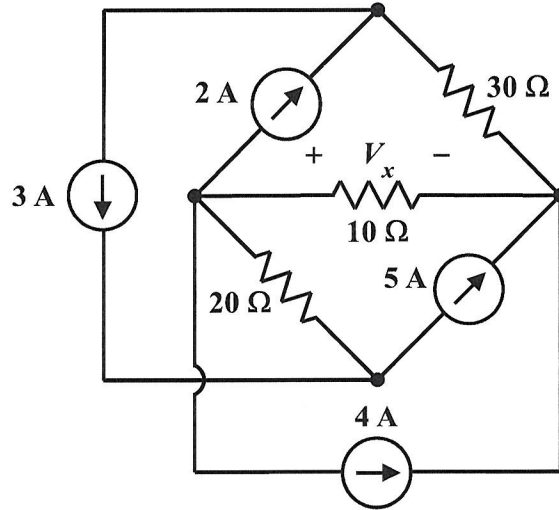


EE 2240
Homework Problem #035

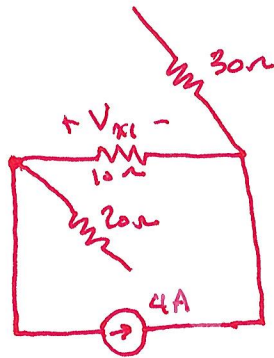


Use the superposition method to determine the value of V_x .

Circuit 1:




$$V_{x1} = -(10\Omega)(4A) = -40V$$

Circuit 2:

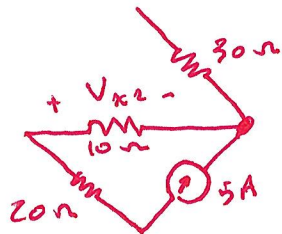


$$V_{x2} = -(10\Omega)(5A) = -50V$$

Circuit 3:

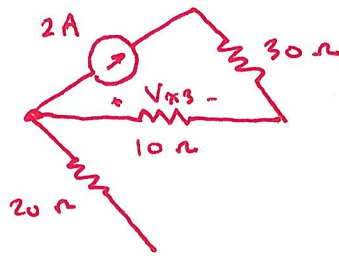

$$V_{x3} = -(10\Omega)(2A) = -20V$$

Circuit 4:

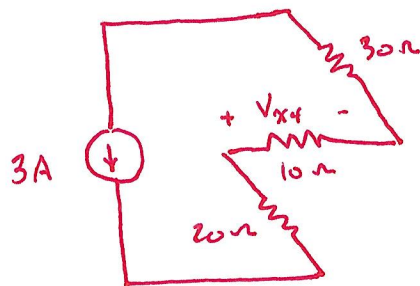

$$V_{x4} = (10\Omega)(3A) = 30V$$

Then

$$\begin{aligned} V_{x5} &= V_{x1} + V_{x2} + V_{x3} + V_{x4} \\ &= -40V - 50V - 20V + 30V \\ &= -80V \end{aligned}$$