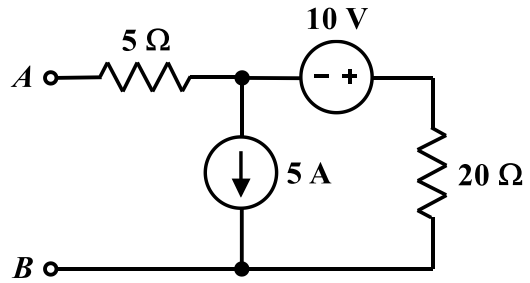


EE 2240  
**Homework Problem #037**



Determine the Norton equivalent circuit with respect to terminals *A* and *B*.