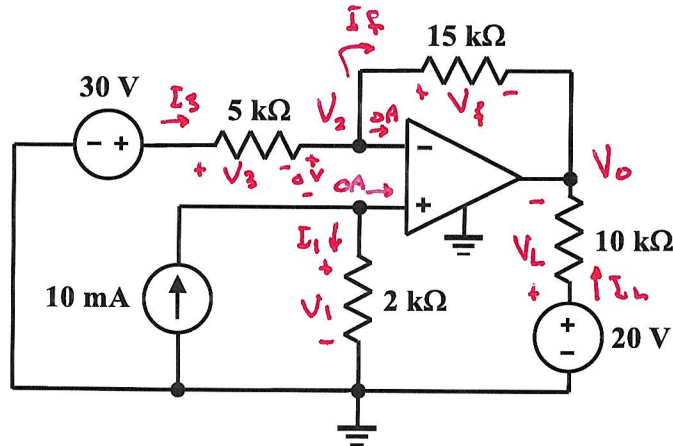


EE 2240  
Homework Problem #042



The OpAmp is ideal.

(a) Determine the amount of power absorbed by the 10 kΩ resistor.

$$I_1 = 10\text{mA} - 0 = 10\text{mA}$$

$$V_1 = (2\text{k}\Omega) I_1 = 20\text{V}$$

$$V_2 = V_1 + 0 = 20\text{V}$$

$$V_3 = 30\text{V} - V_2 - 0 = 10\text{V}$$

$$I_3 = \frac{V_3}{5\text{k}\Omega} = 2\text{mA}$$

$$I_5 = I_3 - 0 = 2\text{mA}$$

$$V_4 = (15\text{k}\Omega) I_5 = 30\text{V}$$

$$V_o = -V_4 + 0 + V_1 = -10\text{V}$$

$$V_L = V_o - 20\text{V} = 30\text{V}$$

$$P = \frac{V_L^2}{10\text{k}\Omega} = 90\text{mW}$$

(b) Is the 20 V source *delivering power* or *absorbing power*? How much?

$$I_L = \frac{V_L}{10\text{k}\Omega} = 3\text{mA}$$

Since  $I_L$  flows out of the "+" end of the source, it is delivering

$$(20\text{V})(I_L) = 60\text{mW}$$