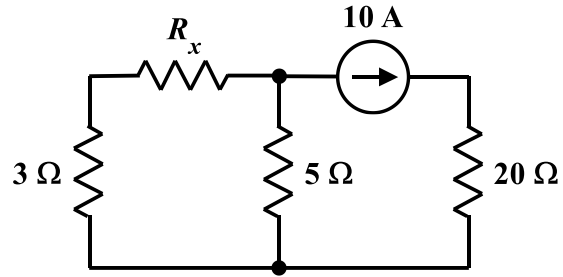


EE 2240
Homework Problem #043



What value of R_x will absorb maximum power from the remainder of the circuit?