
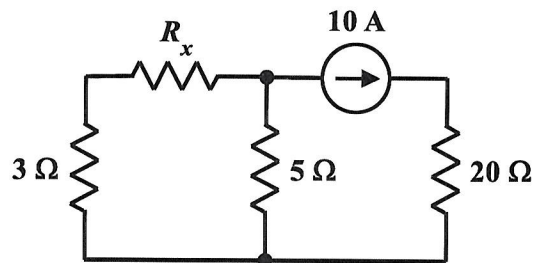


EE 2240
Homework Problem #043

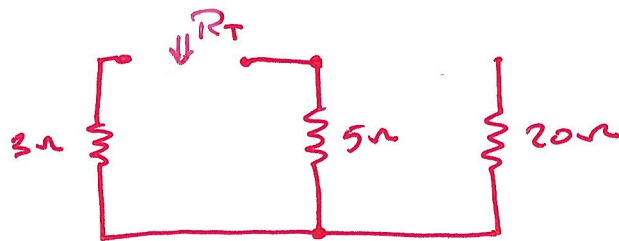

What value of R_x will absorb maximum power from the remainder of the circuit?

Choose R_x equal to the Thévenin equivalent resistance:
w.r.t. the load terminals:



$$R_T = 3\ \Omega + 5\ \Omega = 8\ \Omega$$

$$\therefore \text{choose } R_x = 8\ \Omega$$