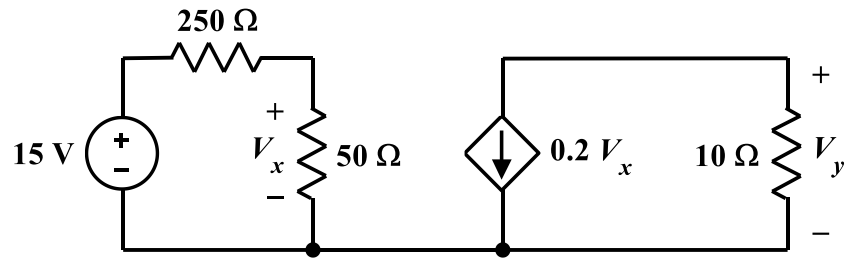


EE 2240
Homework Problem #044



Determine the value of V_y .