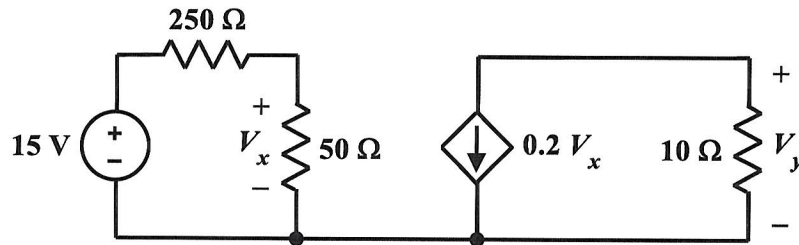


EE 2240
Homework Problem #044



Determine the value of V_y .

$$V_x = \frac{50\Omega}{50\Omega + 250\Omega} (15V) = \frac{1}{6} (15V) = 2.5V$$

$$V_y = -0.2 V_x (10\Omega) \\ = -5V$$