
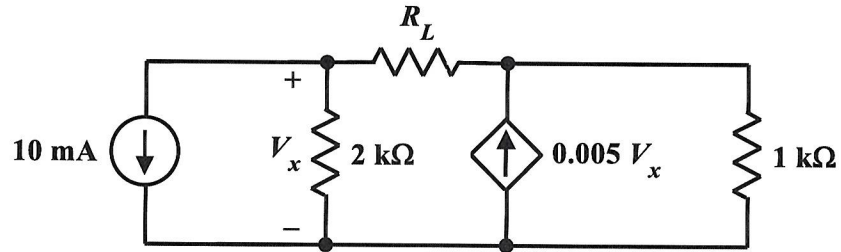


EE 2240
Homework Problem #045

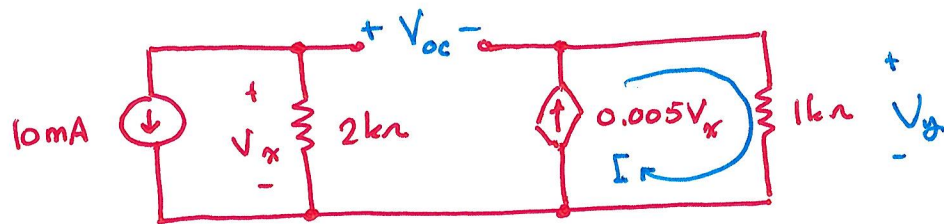

What value of R_L will absorb maximum power from the remainder of the circuit?

Under open-circuit conditions:




$$V_x = -(2\text{k}\Omega)(10\text{mA}) = -20\text{V}$$

$$I = 0.005 V_x = 0.005(-20) = -0.1\text{A}$$

$$V_y = (1\text{k}\Omega) I = -100\text{V}$$

$$V_{oc} = V_x - V_y = -20\text{V} - (-100\text{V}) = 80\text{V}$$

Under short-circuit conditions:

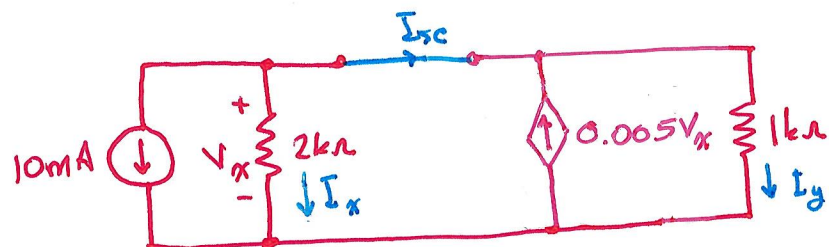

$$I_x = \frac{V_x}{2k\Omega}$$

$$I_y = \frac{V_x}{1k\Omega}$$

$$10mA + I_x - 0.005V_x + I_y = 0 \quad (\text{KCL})$$

$$\text{or } 10mA + \frac{V_x}{2k\Omega} - 0.005V_x + \frac{V_x}{1k\Omega} = 0$$

$$\Rightarrow \left(\frac{1}{2000} - \frac{5}{1000} + \frac{1}{1000} \right) V_x = -10mA$$

$$\text{or } -\frac{7}{2000} V_x = -10mA$$

$$\Rightarrow V_x = \frac{2000}{7} (10 \times 10^{-3}) = \frac{20}{7} V$$

$$\begin{aligned} \text{Then } I_{sc} &= -10mA - I_x \\ &= -10mA - \frac{20/7}{2k\Omega} \\ &= -\frac{80}{7} mA \end{aligned}$$

$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{80}{-\frac{80}{7} \times 10^{-3}} = -\frac{1000}{7} \Omega$$

Controlled sources can make a circuit behave as if it includes a negative resistance!

Since resistors absorb power only if they satisfy the P.S.C., we must choose $R_L = 0$ so that it absorbs 0 watts.