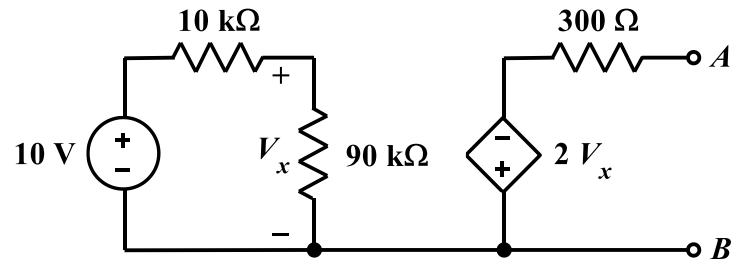


EE 2240

**Homework Problem #048**



Find the Thévenin equivalent circuit with respect to terminals  $A$  and  $B$ .