
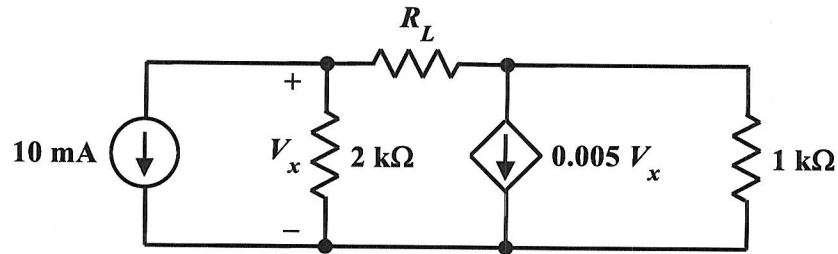


EE 2240  
Homework Problem #049

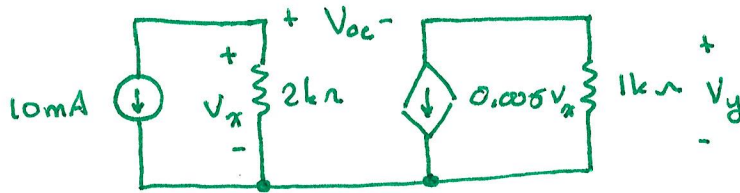


What value of  $R_L$  will absorb maximum power from the remainder of the circuit?



$$V_x = -(2\text{ k}\Omega)(10\text{ mA}) = -20\text{ V}$$

$$V_y = -(1\text{ k}\Omega)(0.005 V_x) = 100\text{ V}$$

$$V_{oc} = V_x - V_y = -120\text{ V}$$

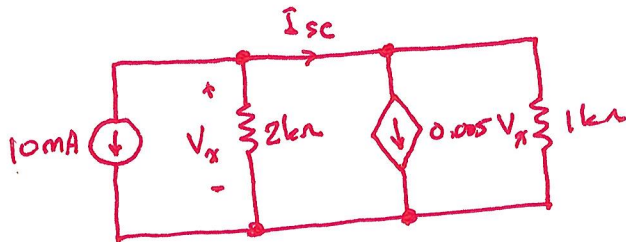

$$10\text{ mA} + \frac{V_x}{2\text{ k}\Omega} + 0.005 V_x + \frac{V_x}{1\text{ k}\Omega} = 0$$

$$\Rightarrow V_x = -\frac{20}{13}\text{ V}$$

$$I_{sc} = -10\text{ mA} - \frac{V_x}{2\text{ k}\Omega}$$

$$= -\frac{120}{13}\text{ mA}$$

$$R_T = R_N = \frac{V_{oc}}{I_{sc}} = \frac{-120\text{ V}}{-\frac{120}{13}\text{ mA}} = 13\ \Omega$$

$$\text{Choose } R_L = R_T = R_N = 13\ \Omega$$