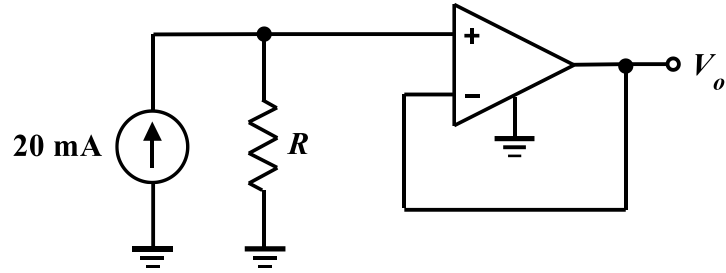


EE 2240  
**Homework Problem #051**



The OpAmp is ideal. Determine the value of  $R$  required to make  $V_o = 10\text{ V}$ .