 


EE 2240
Homework Problem #061

Use LTspice to determine the value of V_x .



Submit a printed copy of your netlist and a printed copy of your output. Highlight the required result.