 


EE 2240
Homework Problem #063

Use LTspice to determine the value of V_o .



Use the LM741/NS model for the OpAmp.

Submit a printed copy of your netlist and a printed copy of your output. Highlight the required result.