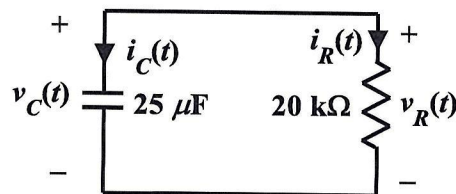


## Homework Problem #064

The capacitor is initially charged so that  $v_C(0) = 4 \text{ V}$ .



- a. Determine the time constant,  $\tau$ , for this circuit.

$$\tau = RC = (20 \text{ k}\Omega)(25 \mu\text{F}) = 0.5 \text{ s}$$

- b. Determine  $v_C(t)$  for  $t \geq 0$ .

$$v_C(t) = v_C(0) e^{-t/\tau} = 4 e^{-2t} \text{ V}$$

- c. Determine  $i_C(t)$  for  $t \geq 0$ .

$$i_C(t) = C \frac{dv_C}{dt} = (25 \mu\text{F})(-2) 4 e^{-2t} = -200 e^{-2t} \mu\text{A}$$

- d. Determine  $v_R(t)$  for  $t \geq 0$ .

$$v_R(t) = v_C(t) = 4 e^{-2t} \text{ V}$$

- e. Determine  $i_R(t)$  for  $t \geq 0$ .

$$i_R(t) = \frac{v_R(t)}{R} = \frac{4 \text{ V}}{20 \text{ k}\Omega} e^{-2t} = 200 e^{-2t} \mu\text{A}$$

- f. Determine the power absorbed by the resistor,  $p_R(t)$ , for  $t \geq 0$ .

$$p_R(t) = R i_R^2(t) = (20 \text{ k}\Omega) [200 e^{-2t} \mu\text{A}]^2 = 800 e^{-4t} \mu\text{W}$$

- g. Determine the charge,  $q(t)$ , stored in the capacitor for  $t \geq 0$ .

$$q(t) = C v_C(t) = 100 e^{-2t} \mu\text{C}$$

- h. What is the final value, [i.e.,  $\lim_{t \rightarrow \infty} q(t)$ ], of the charge stored in the capacitor?

$$\lim_{t \rightarrow \infty} [100 e^{-2t} \mu\text{C}] = 0$$

- i. Approximately how long will it take for the capacitor charge to fall 99% of the way from its initial value to its final value?

$$5\tau = 5(0.5 \text{ s}) = 2.5 \text{ s}$$

- j. What is the value of  $q(t)$  at that point in time?

$$q(2.5 \text{ s}) = 100 e^{-2(2.5)} \mu\text{C} \approx 674 \text{ nC}$$