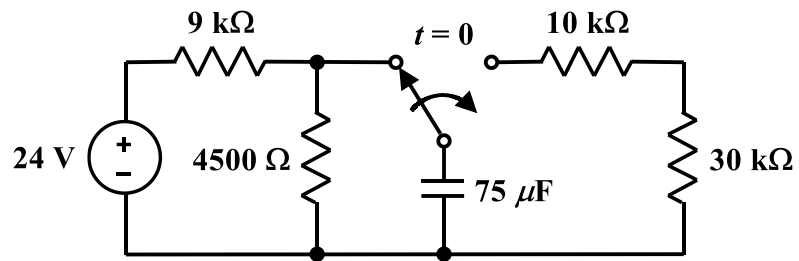


EE 2240
Homework Problem #066



The circuit has reached the DC steady state prior to $t = 0$. Determine the power absorbed by the $10 \text{ k}\Omega$ resistor for $t \geq 0$.