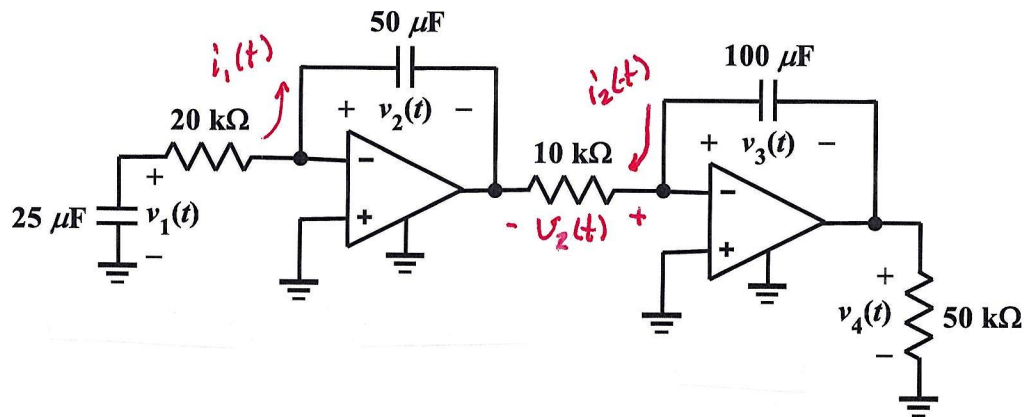


Homework Problem #068



The operational amplifiers are ideal. If $v_1(0) = 20\text{ V}$, $v_2(0) = -10\text{ V}$ and $v_3(0) = -5\text{ V}$, determine $v_4(t)$ for $t \geq 0$.

$$\tau = (20\text{ k}\Omega)(25\text{ }\mu\text{F}) = 0.5\text{ s}$$

$$v_1(t) = 20e^{-2t}\text{ V}, t \geq 0$$

$$i_1(t) = \frac{v_1(t)}{20\text{ k}\Omega} = e^{-2t}\text{ mA}, t \geq 0$$

$$\begin{aligned} v_2(t) &= v_2(0) + \frac{1}{50\text{ }\mu\text{F}} \int_0^t i_1(t) dt \\ &= -10 + 20000 \left[-\frac{1}{2} e^{-2t} \times 10^{-3} \right]_0^t \\ &= -10 - 10 [e^{-2t} - e^0] = -10e^{-2t}\text{ V}, t \geq 0 \end{aligned}$$

$$i_2(t) = \frac{v_2(t)}{10\text{ k}\Omega} = -e^{-2t}\text{ mA}, t \geq 0$$

$$\begin{aligned} v_3(t) &= v_3(0) - \frac{1}{100\text{ }\mu\text{F}} \int_0^t i_2(t) dt \\ &= -5 - 10000 \left[\frac{1}{2} e^{-2t} \times 10^{-3} \right]_0^t \\ &= -5 - 5 [e^{-2t} - e^0] = -5e^{-2t}\text{ V}, t \geq 0 \end{aligned}$$

$$v_4(t) = -v_3(t) = 5e^{-2t}\text{ V}, t \geq 0$$