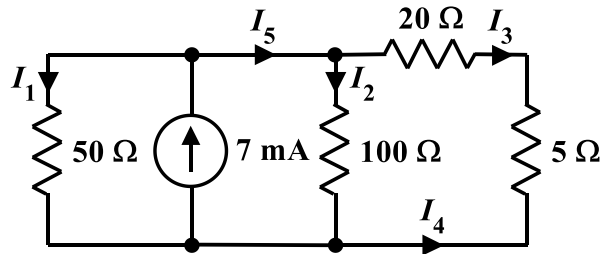


EE/EET 2240
Homework Problem #009



- Use the current divider equation to determine I_1 .
- Use the current divider equation to determine I_2 .
- Use the current divider equation to determine I_3 .
- Determine the value of I_4 .
- Determine the value of I_5 .