

EE/EET 2240

Homework Problem #011

Develop node equations and express them in the matrix form discussed in class. Note that the resistors are specified in conductance units.

