

EE/EET 2240  
**Homework Problem #012**

Determine the value of  $V_o$ .

