

EE/EET 2240
Homework Problem #016

Determine the value of V_x .

