

EE/EET 2240  
**Homework Problem #019**

Determine the amount of power absorbed by the 12k $\Omega$  resistor.

