

Homework Problem #019

X and Y are linear components. If $I_0 = 15$ mA when $V_s = 60$ V, what will be the new value of I_0 if V_s is decreased to 20 V?

