

EE/EET 2240  
**Homework Problem #020**

Use the nodal analysis method to determine the voltage,  $V$ , across the 4 siemens conductance.

