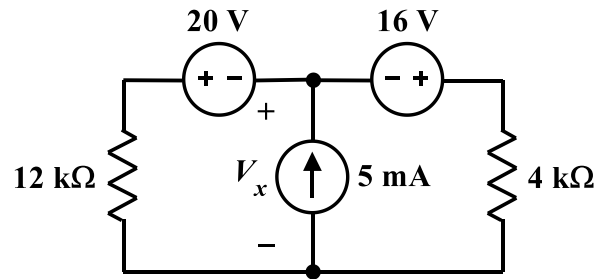


EE/EET 2240
Homework Problem #021



Use the superposition method to determine the value of V_x .