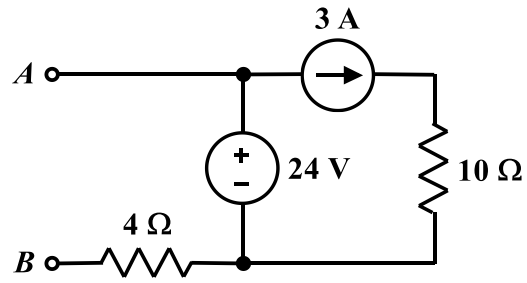


EE/EET 2240  
**Homework Problem #026**



Find the Norton equivalent circuit with respect to terminals *A* and *B*.