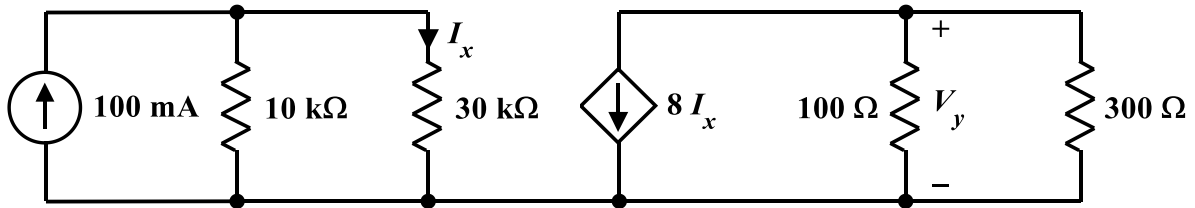


EE/EET 2240
Homework Problem #029



(a) Determine the value of V_y .

(b) Does the CCCS *absorb* or *deliver* power? How much?