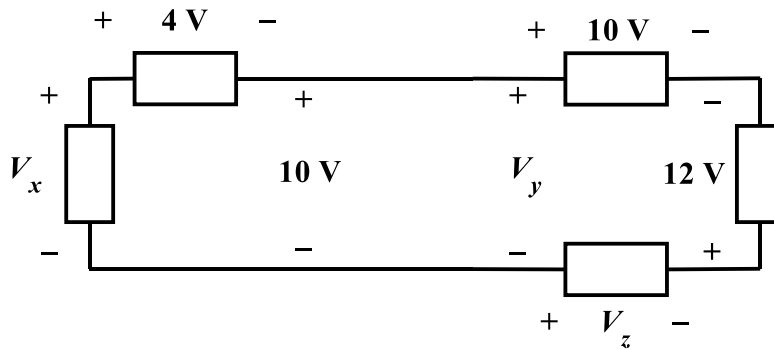


EE/EET 2240
Homework Problem #03

For the circuit shown below:



- a. How many nodes does the circuit have?

- b. How many branches (components) make up the circuit?

- c. Determine the value of V_x .

- d. Determine the value of V_y .

- e. Determine the value of V_z .