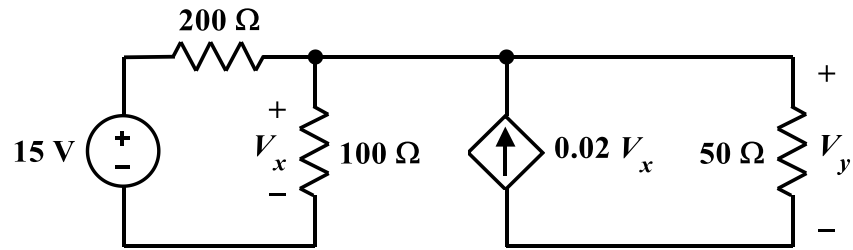


EE/EET 2240
Homework Problem #030



(a) Determine the value of V_y .

(b) Does the VCCS *absorb* or *deliver* power? How much?