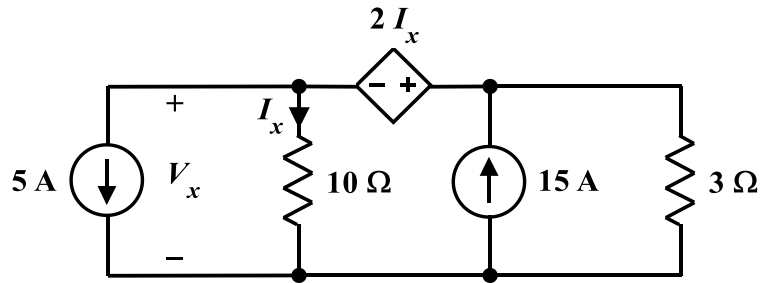


EE/EET 2240
Homework Problem #031



Determine the value of V_x .