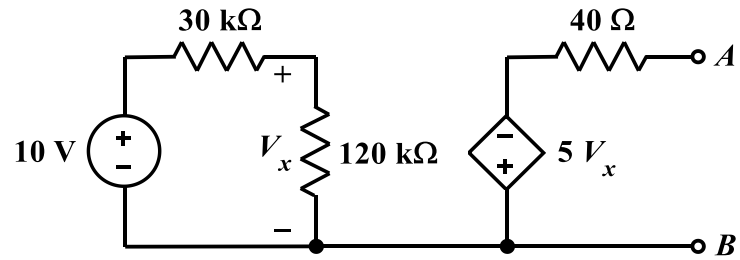


EE/EET 2240
Homework Problem #032



Find the Norton equivalent circuit with respect to terminals A and B.