

EE/EET 2240
Homework Problem #034

Use a netlist and PSpice to determine numerical values for the current I_x and the voltage V_z . Both should specifically appear in the output file. Highlight them in some obvious manner on the printout you submit for grading.

