

EE/EET 2240

Homework Problem #035

Determine the value of I_o using linearity/proportionality and the initial assumption that $I_o = 1 \text{ mA}$.

