

EE/EET 2240  
**Homework Problem #037**

Determine the value of  $I_o$  using superposition.

