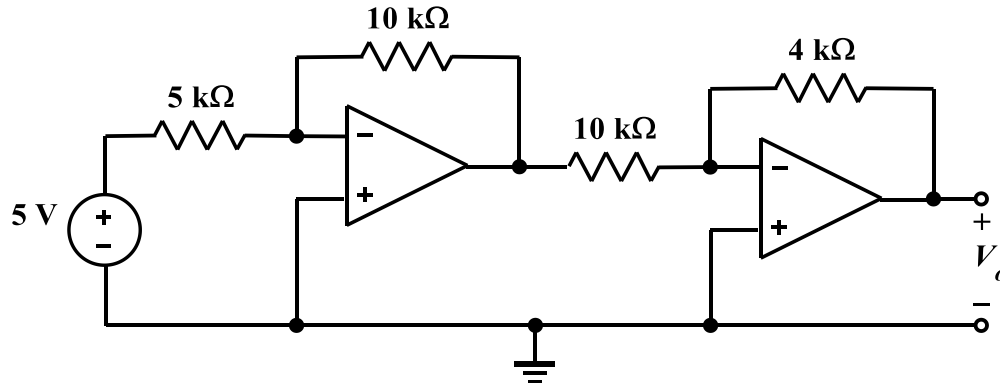


EE/EET 2240
Homework Problem #037



The OpAmps are ideal. Determine the value of V_o .