

Homework Problem #039

Treating the $4\text{ k}\Omega$ resistor as the load, use source transformations to reduce the remainder of the circuit to the point where you can apply the voltage divider principle to determine the value of V_o .

