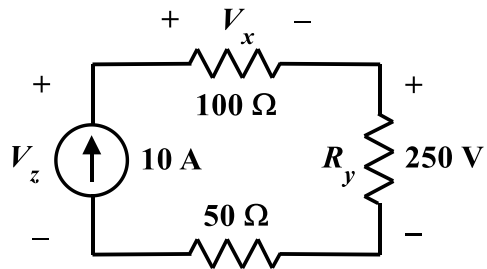


EE 2240
Homework Problem #05

For the circuit shown below:



- Determine the value of V_x .
- Determine the value of R_y .
- Determine the value of V_z .
- How much power does R_y absorb?
- How much power does the independent current source deliver?