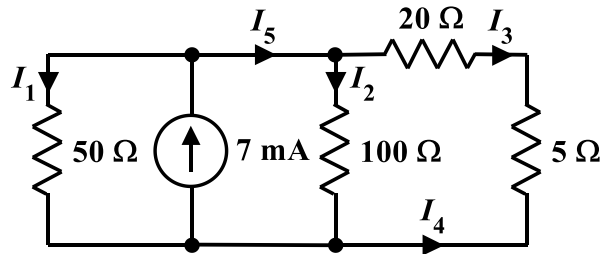


EE 2240  
**Homework Problem #09**



- Use the current divider equation to determine  $I_1$ .
- Use the current divider equation to determine  $I_2$ .
- Use the current divider equation to determine  $I_3$ .
- Determine the value of  $I_4$ .
- Determine the value of  $I_5$ .