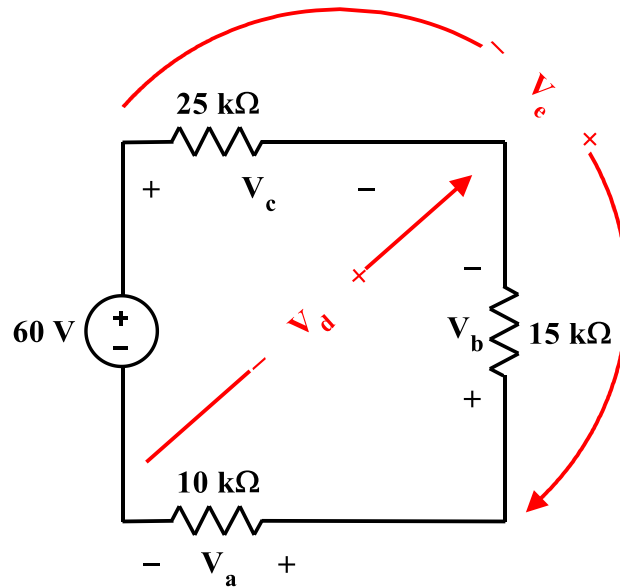


EE/EET 2240
Homework Problem #09



- Use the voltage divider equation to determine the value of V_a .
- Use the voltage divider equation to determine the value of V_b .
- Use the voltage divider equation to determine the value of V_c .
- Use any method to determine the value of V_d .
- Use any method to determine the value of V_e .