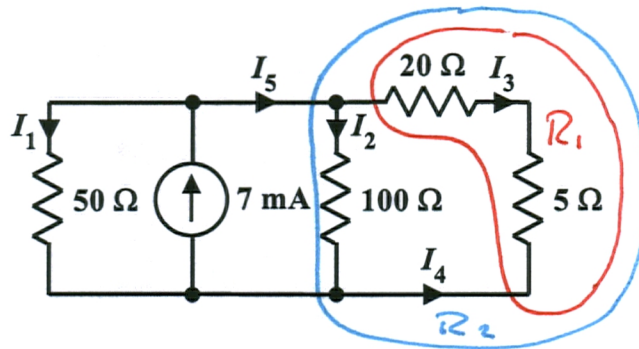


EE 2240
Homework Problem #09



$$R_1 = 20\Omega + 5\Omega = 25\Omega$$

$$R_2 = 100\Omega \parallel R_1$$

$$= \frac{1}{\frac{1}{100} + \frac{1}{25}} = 20\Omega$$

- a. Use the current divider equation to determine I_1 .

$$I_1 = \frac{\frac{1}{50\Omega}}{\frac{1}{50\Omega} + \frac{1}{R_2}} (7\text{mA}) = 2\text{mA}$$

- b. Use the current divider equation to determine I_2 .

$$I_2 = \frac{\frac{1}{100\Omega}}{\frac{1}{50\Omega} + \frac{1}{100\Omega} + \frac{1}{R_1}} (7\text{mA}) = 1\text{mA}$$

- c. Use the current divider equation to determine I_3 .

$$I_3 = \frac{\frac{1}{R_1}}{\frac{1}{50\Omega} + \frac{1}{100\Omega} + \frac{1}{R_1}} (7\text{mA}) = 4\text{mA}$$

- d. Determine the value of I_4 .

$$I_4 = -I_3 = -4\text{mA}$$

- e. Determine the value of I_5 .

$$I_5 = I_2 + I_3 = 5\text{mA}$$